

CMOS buffer delivers precise current pulses

HARTMUT HENKEL, CONSULTANT, KRIFTTEL, GERMANY

The circuit in Fig 1 delivers stable, fast-settling reference-current pulses. You can use the circuit in systems employing A/D, D/A, or V/F converters.

Digital input pulses, V_P , connect to IC_{3B} , a 74AC240 buffer. The 5.00V reference, IC_1 , constrains IC_{3B} 's output, V_R , to either V_{REF} or 0V. IC_{3B} 's rise and fall times are <3 nsec. Resistor R_1 converts the voltage at the output of IC_{3B} to a current: $I_R = V_R/R_1$. I_R flows into integrator IC_4 's virtual ground.

An analog control loop comprising IC_2 and IC_{3A} stabilizes V_{REF} . The loop compensates for the 20 Ω output resistance of buffer IC_{3B} . And, the loop reduces high-frequency noise from reference IC_1 (Ref 1). Diode D_1 prevents reverse polarity during power-up.


You should use tantalum capacitors for C_1 and C_2 . Locate C_2 as close as possible to IC_3 's supply pins. If you use a low-temperature-coefficient Vishay (Malvern, PA, (610) 644-1300) resistor for R_1 and select 100 k Ω as the values for R_1 , R_2 , and R_3 , IC_1 is the source of most of your current drift. (DI # 1635) EDN

Reference

1. Application note AB-003, Burr-Brown Corp, Tucson, AZ. (602) 746-1111.

To Vote For This Design, Circle No. 343

FIGURE 1

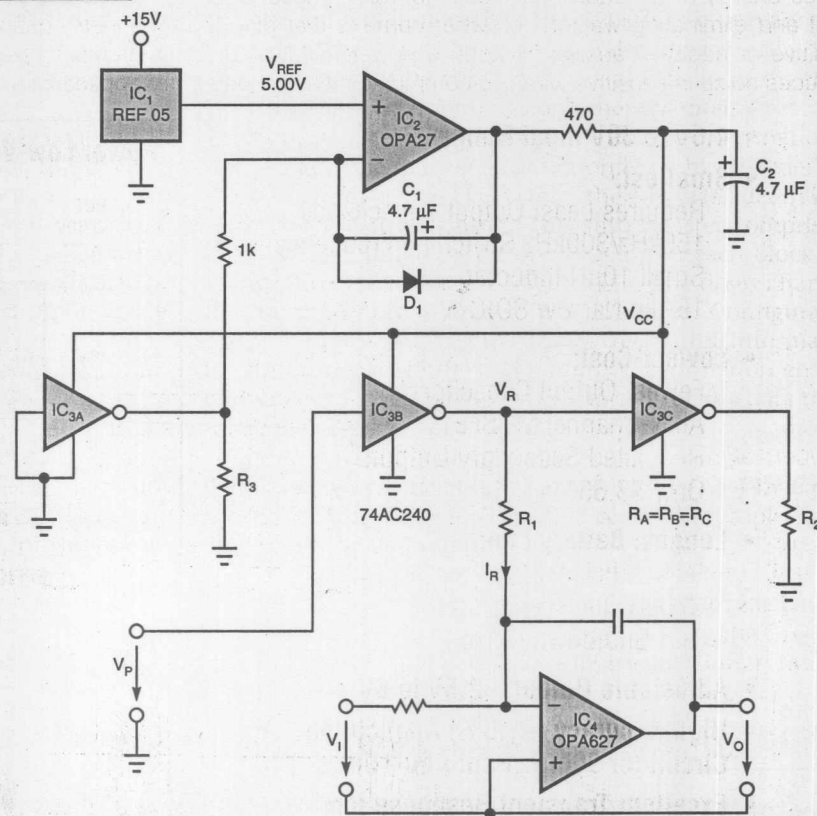

This circuit delivers stable, fast-settling reference-current pulses because of its stable components and controlled-voltage level.

Repeating one-shot yields clean, stable pulses

PHIL HARVEY, TECHNOLOGY INTEGRATION, BEDFORD, MA

Now and then, you need a repeating one-shot, such as a multi-shot. For example, when an input logic signal or alarm condition occurs, you may need an immediate pulse to provoke a sequence that eventually resets the condition. But, if the resetting fails, you need to keep generating pulses until the message gets through. If you give up sending pulses, something as important as an entire space mission could have to wait for an automatic reset.


Although you can generate multiple reset pulses many ways, most methods are fraught with annoyances. The first pulse can be twice as long as the follow-on pulses. Or, as for the retriggerable one-shot, keeping the pulse generator on

prolongs the pulse instead of making new ones. When turned off, the pulse generator sometimes cuts the last output pulse off, hatching short glitches.

The circuits in Fig 1a and 1b are gated Schmitt oscillators. The oscillators respond to a negative input by producing a pulse of fixed length, regardless of how long the input stays on. The oscillators refuse to operate for a certain period. If the input is still there, the devices produce another pulse of the same fixed length.

In its quiescent state, the signal at the junctions is high (Fig 1a). C_1 couples the high-going transient to the diodes when the output toggles. The diodes clip the signal to 0.6V

FLASH Solutions for embedded systems

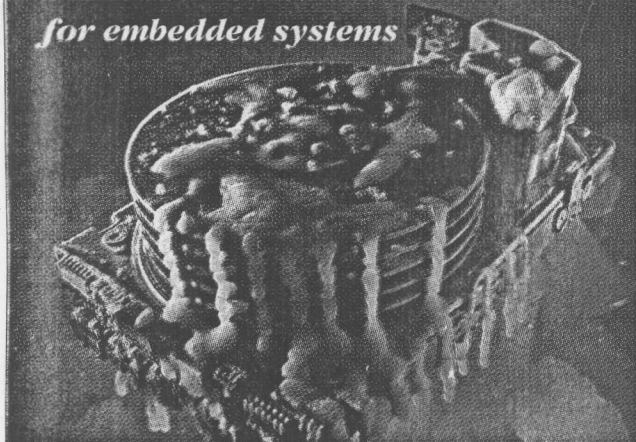

Do you need a Solid-State Disk?

M-Systems has a complete, off-the-shelf solution:

- ▶ 100% hard disk emulation - Bootable
- ▶ ISA, PC-104 interface
- ▶ Up to 32 MB uncompressed (up to 64 MB compressed)
- ▶ No additional design required

Now with more attractive prices

M-Systems
Flash Disk Pioneers

Israel
Tel: 972-3-647-7776
Fax: 972-3-647-6668

USA
Tel: 408-654-5820
Fax: 408-654-9107


The Netherlands
Tel: 31-10-262-1144
Fax: 31-10-462-4855

CIRCLE NO. 102

SUPER TURBO ROM-IT™ Championship Edition

The MOST Flexible EPROM
Emulator You Can Get Today!

Now
4 Times
FASTER!

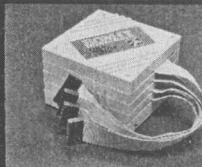

Windows
and DOS
Versions
INCLUDED!

Emulates up to eight 4-Megabit
EPROMs from one serial port.

- Download 4 Megabits in 11.6 seconds!
- Standard access time of 100 nanoseconds (faster speeds are available)
- Easily Expandable!
- Accepts Intel Hex, Motorola S-record and Binary files.
- Base system starting at \$395. Other configurations available.



Order your ROM-IT Today!
Incredible Technologies, Inc.
Call (708) 870-7027 or FAX (708) 870-0120
Visa, Mastercard, and American Express Accepted

CIRCLE NO. 88

EDN

DESIGN IDEAS

above the positive rail. A relaxation cycle begins as C_1 's charge drains away, and its voltage heads for the Schmitt trigger's lower threshold.


When the circuit receives a continuous input signal, each subsequent relaxation cycle starts with the diodes driven high. The diodes start high, even through C_1 's voltage decays to the upper Schmitt level during the output pulse's on period. So, the circuit generates almost exactly the same pulse length every time, including the first time.

Fig 1b's circuit, the simpler of the two versions, lacks clamping diodes and a transistor. The circuit's first pulse is slightly longer because the transition starts at a higher voltage. Fig 1b's circuit is a trifle less temperature-stable than Fig 1a's. (DI #1636)

EDN

To Vote For This Design, Circle No. 344

FIGURE 1

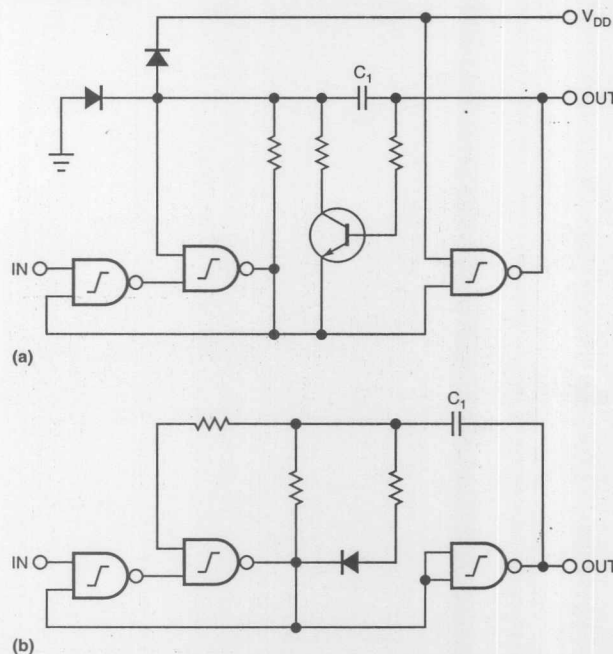

The gated Schmitt pulse generators in (a) and (b) respond to a negative input by producing a train of pulses of the same length.

How to use our bulletin board



This icon identifies those Design Ideas that have computer-readable material posted on EDN's bulletin-board system (BBS). Call our free BBS at (617) 558-4241 (325/1225/2425 8,N,1). Not every Design Idea has downloadable material, but each one does have a BBS number printed at the end of it. If you'd like to comment on any Design Idea, include the number in the subject field of your message.

INTUWAC
6th

Distrib
Californ
GA, En
Comp, I
Corpora
Corpora
Represe
Distrib
Austria
Maxim
Koning
Electro